

Assignment 4

AI1110: Probability and Random Variables
Indian Institute of Technology Hyderabad

K S Ananth
CS22BTECH11029

Abstract—In this assignment we have made a Random number generator using shift registers

- (ii) Then we connected Clock output of 555 timer circuit to the clock signal of D-Flip flops
- (iii) Now we make the circuit for shift registers using a 4 D-Flip flops (using two 7474 IC's)

1 COMPONENTS USED

Component	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1 K Ω	1
Capacitor	100 nF	1
Capacitor	10 nF	1
Jumper Wires		

TABLE 0: Components used

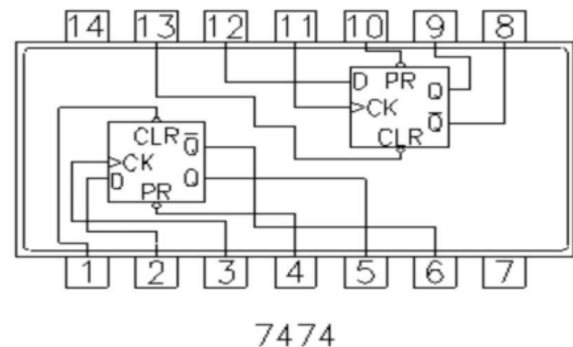


Fig. (iii): Connection in 7474 IC

2 PROCEDURE

- (i) We connected the 555 timer circuit according to the figure (i)

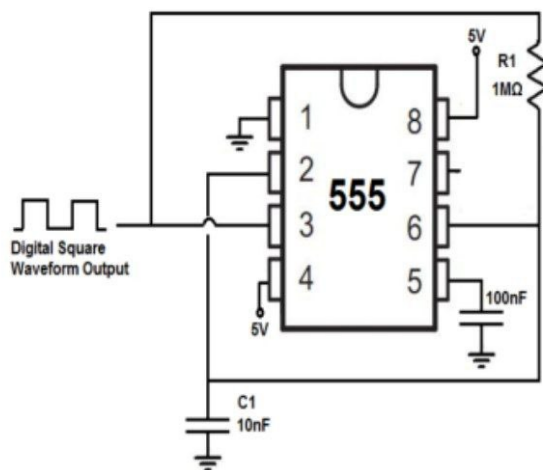


Fig. (i): Connection in 555 timer circuit

- (iv) Then we connected XOR gate (7486 IC) according to the figure (iv)

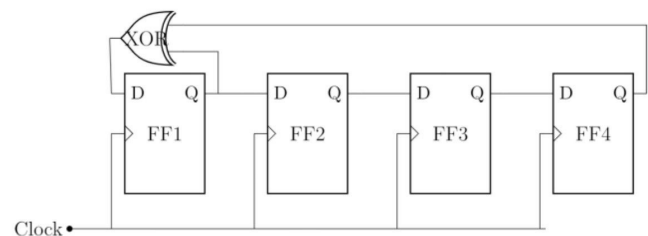


Fig. (iv): Connection in XOR gate

- (v) then we connected the decoder (7447 IC) and connected its A,B,C,D with Q_0, Q_1, Q_2, Q_3 respectively as per the figure (v)
- (vi) Then we connected The seven segmented display and then connected it with the dceoder (7447 IC) according to the table (vi) and the figure (vi)



Fig. (v): Connection in Decoder gate

7447	\bar{a}	\bar{b}	\bar{c}	\bar{d}	\bar{e}	\bar{f}	\bar{g}
Display	a	b	c	d	e	f	g

Fig. (vi): Connection of seven segmented display with decoder

- (vii) We connected all the independent parts with each other and then connected the power source

3 OUTPUT

Output was changing digits on the seven segment display the output is shown in figure (vii)

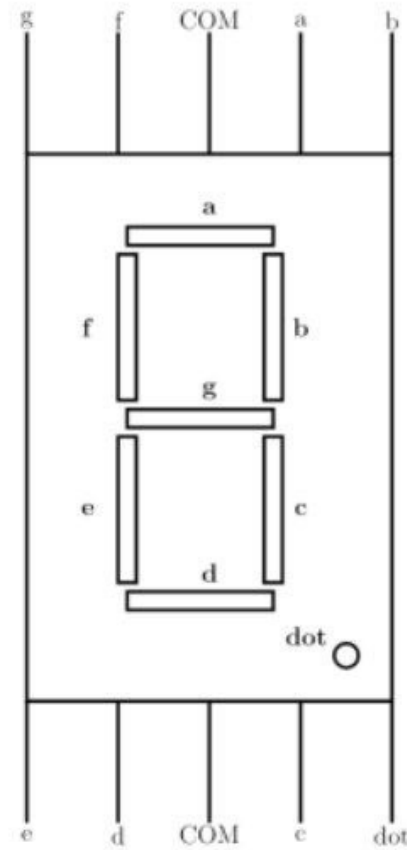


Fig. (vi): Seven segmented display

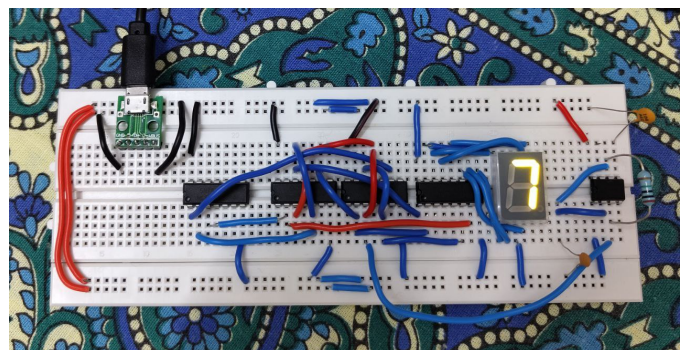


Fig. (vii): output